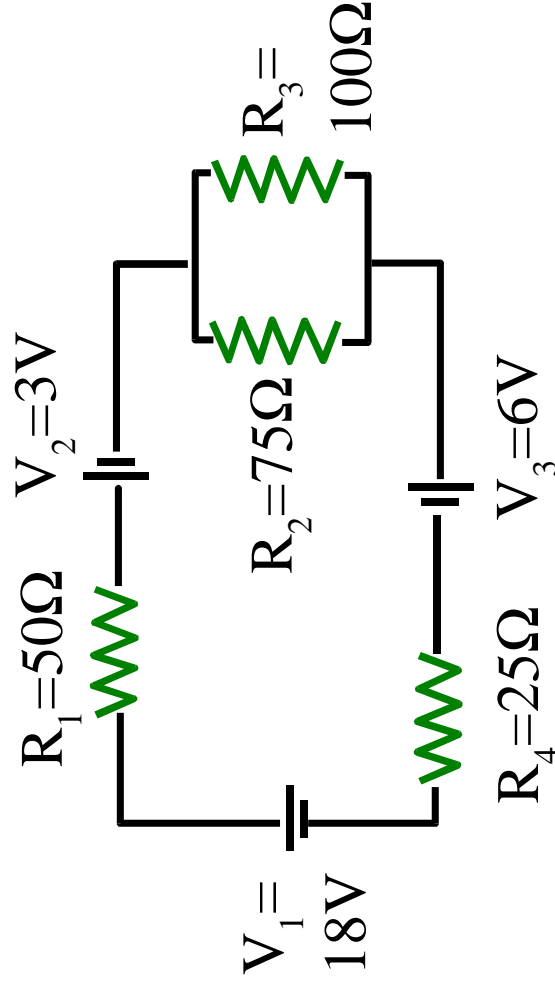



# More Complicated Circuits



What happens if you have a much more complicated circuit? The circuit has 3 sources of emf (3 batteries),  $R_2$  and  $R_3$  are two resistors in parallel, and resistors  $R_1$ ,  $R_{23eq}$ , and  $R_4$  are in series.

To solve this, we need to first define the direction of current from each battery. We choose the current to flow from the positive side of the battery and into the negative side. This *convention* dates from the original belief that the current in metals was made from positive charges. We now know it is electrons (negative charges) which flow readily in metals.

# Current Junctions

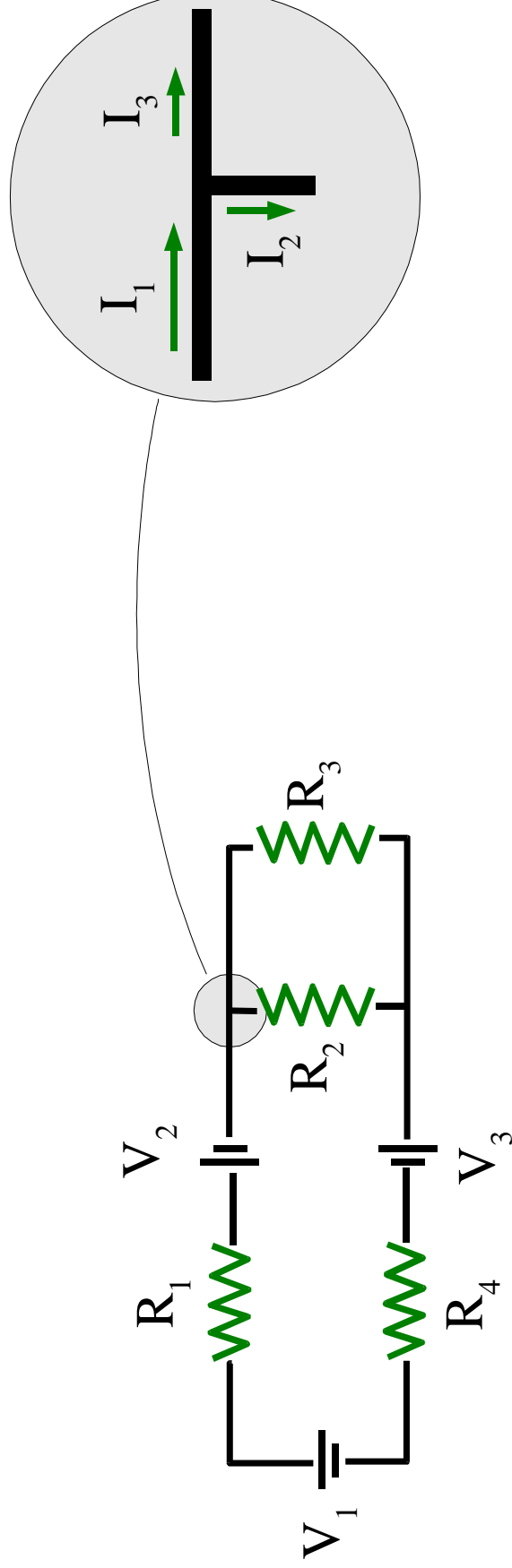


Junctions deal with the current at a point where it can take two different paths. We use conservation of charge to explain this.

This allows one to write one equation for each junction. In this case, the equation is:


$$I_1 = I_2 + I_3$$

# Current Loops

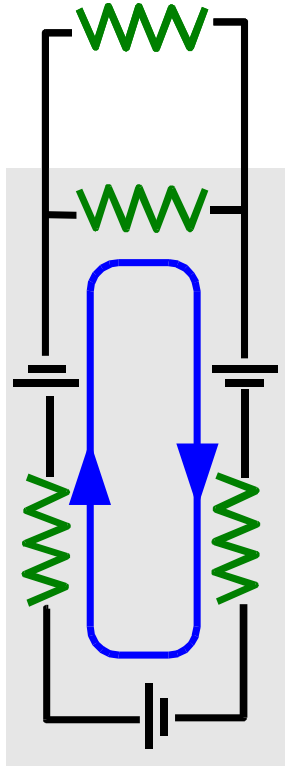

Loop 1

We choose to go around each loop in a clockwise direction. This is an arbitrary choice and the physics would not change if you go the other direction.

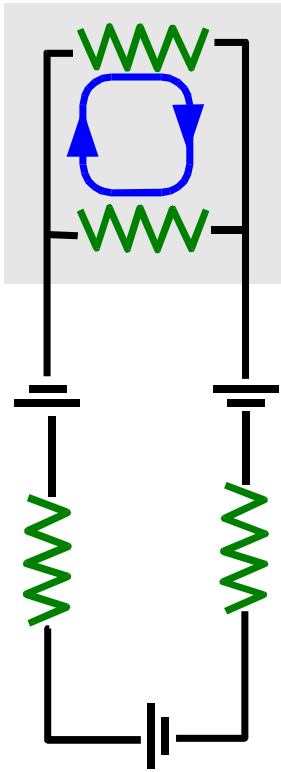


Loop 2

For each loop:


$$\sum \text{Emf} = \sum IR\text{'s}$$

You need to **pay attention** how you **cross a battery** and also the direction you chose for the **current** when you declared your current junction equation.

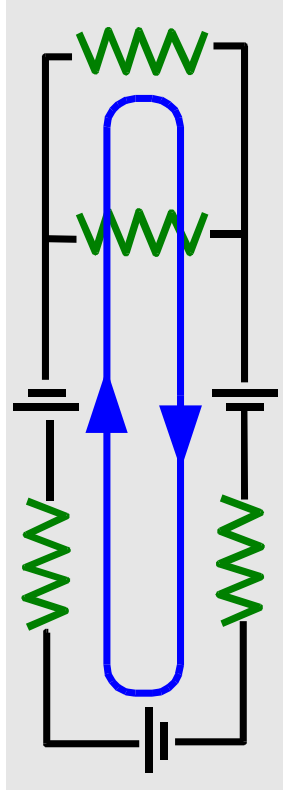

Loop 3

# Loop 1 and Loop 2

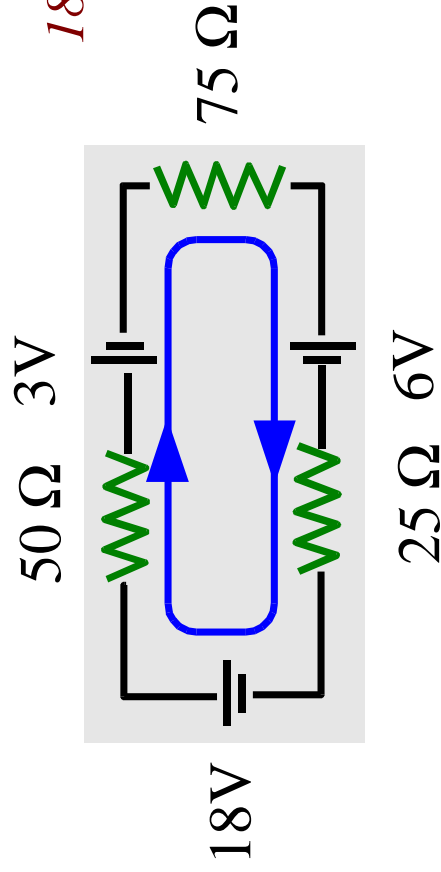


$$\Sigma \text{Emf} = \Sigma IR's$$

$$18V - 3V - 6V = I_1(50\Omega) + I_2(75\Omega) + I_1(25\Omega)$$

$$9 = (50 + 25)I_1 + 75I_2$$

$$9 = 75I_1 + 75I_2$$

25 Ω 6V

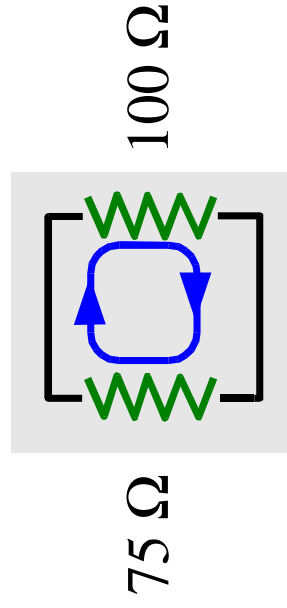

$$\Sigma \text{Emf} = \Sigma IR's$$

$$0V = I_3(100\Omega) - I_2(75\Omega)$$

$$100I_3 = 75I_2$$

$$I_3 = \frac{75}{100}I_2$$

$$I_3 = \frac{3}{4}I_2$$

# Solve the Problem

---

We could solve for loop three as well but we do not need it. We have three equations and only three unknowns:

$$(A) \quad I_1 = I_2 + I_3 \quad (C) \text{ into } (A)$$

$$(B) \quad 9 = 75I_1 + 75I_2 \quad \longrightarrow$$

$$I_1 = I_2 + \frac{3}{4}I_2$$

$$(C) \quad I_3 = \frac{3}{4}I_2$$

$$(D) \quad I_1 = 1.75I_2$$

$$(D) \text{ into } (B) \quad \longrightarrow$$

$$9 = 75(1.75I_2) + 75I_2$$

$$9 = (131.25 + 75.00)I_2$$

$$(E) \quad I_2 = 0.044 \text{ A}$$

$$\longrightarrow$$

$$(E) \text{ into } (C) \quad \longrightarrow$$

$$I_3 = \frac{3}{4}(0.044) \text{ A}$$

$$(F) \quad I_3 = 0.033 \text{ A}$$


$$\longrightarrow (F) \text{ and } (E) \text{ into } (A)$$

$$I_1 = 0.044 \text{ A} + 0.033 \text{ A}$$


$$I_1 = 0.077 \text{ A}$$

# Capacitors in Series and Parallel

---

 

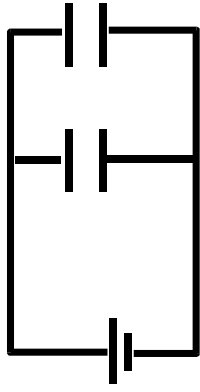When you have capacitors in series, the charge on both sets of plates is equal. The voltage gets split between both capacitors.




When you have capacitors in parallel, the voltage across each capacitor is the same. The charge gets split between the two.
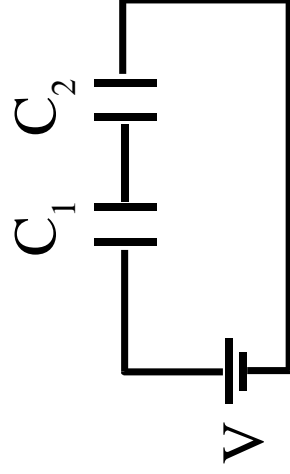
# Capacitors in Series

---

Here, the charge on each plate is the same  
so the total voltage is split between both capacitors.



$$V_T = V_1 + V_2$$

$$\text{Since, } q = CV \Rightarrow V = \frac{q}{C}$$

$$\frac{q}{C_T} = \frac{q}{C_1} + \frac{q}{C_2}$$

therefore


$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

Notice how this is *opposite* resistors in series
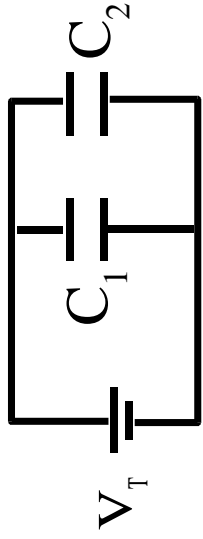
# Capacitors in Parallel

---

Here, the voltage across each capacitor is the same  
so the charge is distributed across both capacitors.



$$q_T = q_1 + q_2$$

$$\text{Since } q = CV$$

$$C_T V = C_1 V + C_2 V$$


therefore

$$C_T = C_1 + C_2$$

Notice how this is the *opposite* to resistors in parallel

# Circuit with both a Resistor and a Capacitor.

---

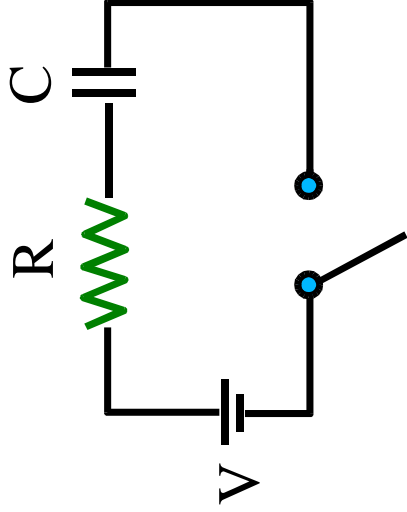

Switch


With the switch open, there is no complete circuit so charge does not flow.

Let's say there is no charge on the capacitor originally. Once the switch is closed, charge flows from the one capacitor plate, across the switch, through the battery, and through the resistor before it is deposited on the second capacitor plate.

Remember that  $I$  (current) is how much charge per time moves through a point in the circuit. Also recall that  $I = V/R$  (Ohm's Law) so we may write:

$$I = \frac{V}{R} \Rightarrow \frac{\Delta q}{\Delta t} = \frac{V}{R} \Rightarrow \Delta q = \frac{V}{R} \Delta t$$

# Capacitor Charging

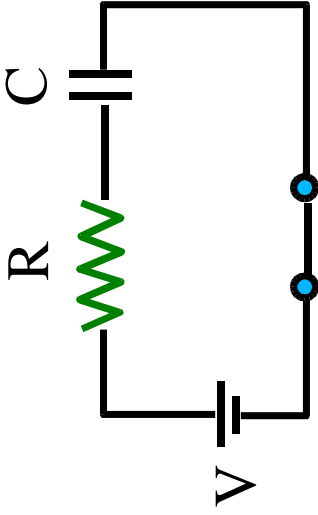

Switch

$$\Delta q = \frac{V}{R} \Delta t$$


but, for any capacitor

$$q = CV \Rightarrow V = \frac{q}{C}$$

$$\Delta q = \frac{q}{RC} \Delta t$$

Solving how the amount of charge on the capacitor plates changes with time, we find (using calculus):
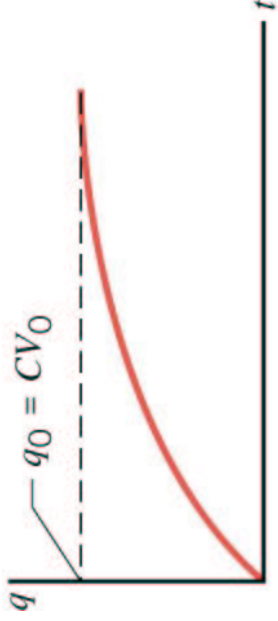
$$q = q_0 \left[ 1 - e^{-t/(RC)} \right]$$



Cutnell & Johnson

Wiley Publishing

Physics 5th Ed.

Figure 20.38 (W784)


CMYK

RC is known as  $\tau$ . This is the time it takes for the capacitor to become 63.2% charged. This is also known as the **characteristic time** of the capacitor.


# Different Resistors Change Charging Time




R=1

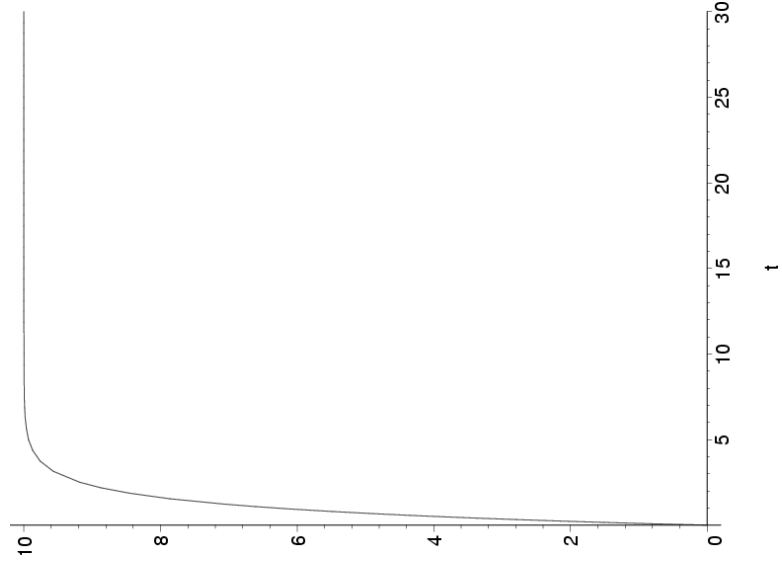


R=5

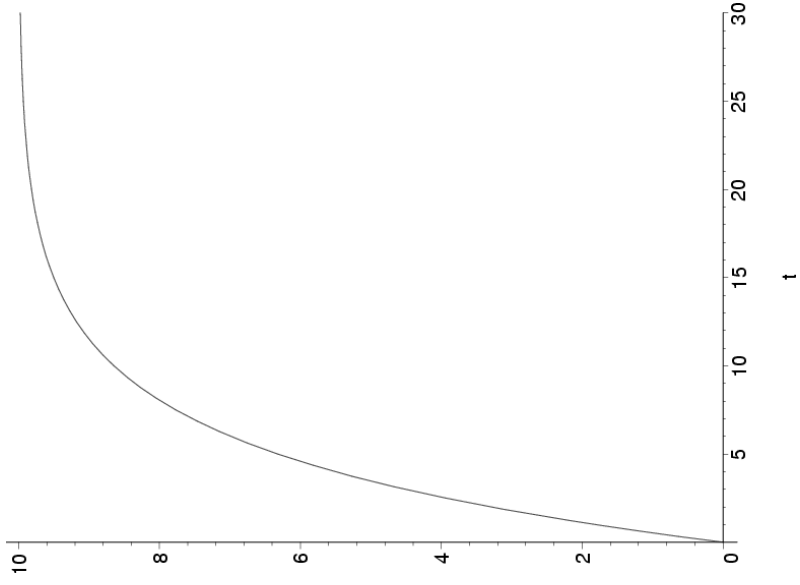

R=10

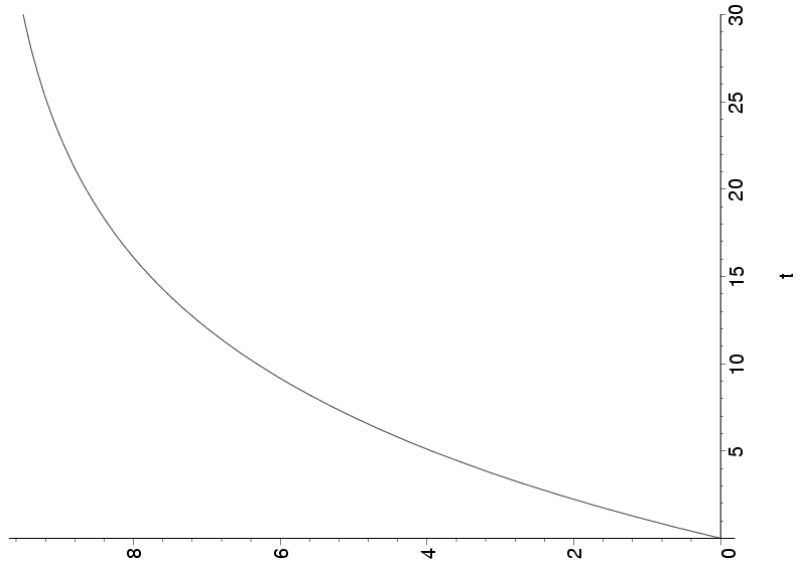

# Capacitor Discharging

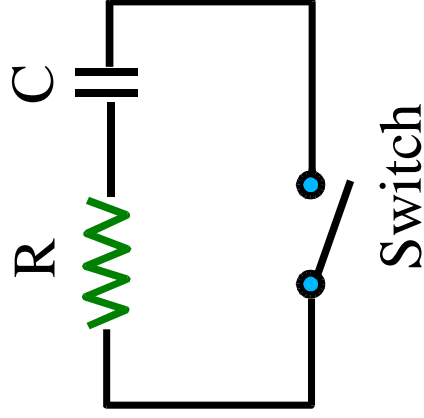

Here you have a case where the capacitor has stored charge and you wish to discharge it. Once the switch is closed, the situation is given by the following equation:

$$q = q_0 e^{-t / RC}$$

Here,  $RC$  or  $\tau$ , is the time it takes the capacitor to lose 63.2% of its charge.

